 


# Chapter 6


1980s-90s

PLA


 
## Muxes and Decoders

Sometimes building blocks of circuit can be larger than simple gates. Having larger building blocks reduces the number of inter-connection switches.




### 6.1 Objectives

1. Design combinational circuits using multiplexers and decoders

### 6.2 Design combinational circuit using multiplexers [1, Section 2.8.1]


 
#### 6.2.1 Review: 2to1 Multiplexer (MUX)



S	Y
0	$D_0$
1	$D_1$

$S_0$	$D_1$	$P_2$	Y
0	0	0	0
0	0	1	0
:	:	:	:
1	1	1	1

S	$D_1$	$D_0$	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

  


$$Y = S D_1 + \bar{S} D_0$$

$$Y = D_0 \bar{S} + D_1 S$$
 
#### 6.2.2 Wider multiplexers

Draw the symbol for a 4:1 MUX, an 8:1 MUX and a  $2^N : 1$  MUX and write corresponding Boolean expressions.




$S_1$	$S_0$	Y
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

$$Y = \underbrace{\bar{S}_1 \bar{S}_0}_{m_0} D_0 + \underbrace{\bar{S}_1 S_0}_{m_1} D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

43



$$2 = \log_2(4)$$

$$2^2 = 4$$


 


$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

$$3 = \log_2(8) \Rightarrow 2^3 = 8$$

  

  Example 6.1. Design a circuit for  $Y = \underline{A\bar{B} + \bar{B}\bar{C} + \bar{A}BC}$  using a 8:1 MUX.



A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

Remark 6.1. A  $2^N : 1$  MUX can be used to program any  $N$ -input logic function.

Example 6.2. Design a circuit for  $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$  using a 4:1 MUX and NOT gates only.

Remark 6.2. A  $2^{N-1} : 1$  MUX can be used to program any  $N$ -input logic function, if we use literals on the input side.

Example 6.3. Design a circuit for  $Y = \bar{A}C + \bar{A}B + B\bar{D}$  using a 8:1 MUX and NOT gates only. Also design using 4:1 MUX and other gates. fewest gates.

Problem 6.1. (15 marks [1, Ex-2.42]) Implement the function  $Y = BC + \bar{A}\bar{B}\bar{C} + B\bar{C}$  using

1. an 8:1 multiplexer
2. a 4:1 multiplexer and no other gates
3. a 2:1 multiplexer, one OR gate, and an inverter

## 6.3 Encoders and Decoders

Example 6.4. Draw the symbol and the truth table for 2:4 decoder. Also write the logic expressions.

**Example 6.5.** Draw the symbol and the truth table for 3:8 decoder, 4:16 decoder and  $N : 2^N$  decoder. Also write the logic expressions.

**Example 6.6.** Design a circuit for a XOR gate using a 2:4 decoder and an OR gate.

**Example 6.7.** Design a circuit for  $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$  using a 3:8 decoder and an OR gate.

### 6.3.1 (Priority) Encoders

**Example 6.8.** Draw symbol and truth table for a 4:2 priority encoder.

**Example 6.9.** Draw symbol and truth table for a 8:3 priority encoder.