



Digital circuit design notes

Vikas Dhiman for ECE275¹

January 24, 2025

¹The notes are from the following books [1, 2]. Not intended for distribution outside the class.

Contents

1	Boolean Algebra	3
1.1	Learning objectives	3
1.2	Motivating Problem	3
1.3	Basic Gates and notations summary	5
1.4	Digital circuits or networks	6
1.5	Two input networks	6
1.6	Multi-input networks	7
1.7	Minterms and Maxterms	8
1.7.1	Minterms	8
1.7.2	Maxterms	10

Chapter 1


Boolean Algebra

1.1 Learning objectives

1. Representing digital circuits
2. Converting between different notations: Boolean expression, logic networks and switching circuits
3. Converting between different logic network specifications: truth table, minterm, maxterms, product of sums canonical form and sum of product canonical form.
4. Introduce truth tables as Behavioral Verilog

1.2 Motivating Problem

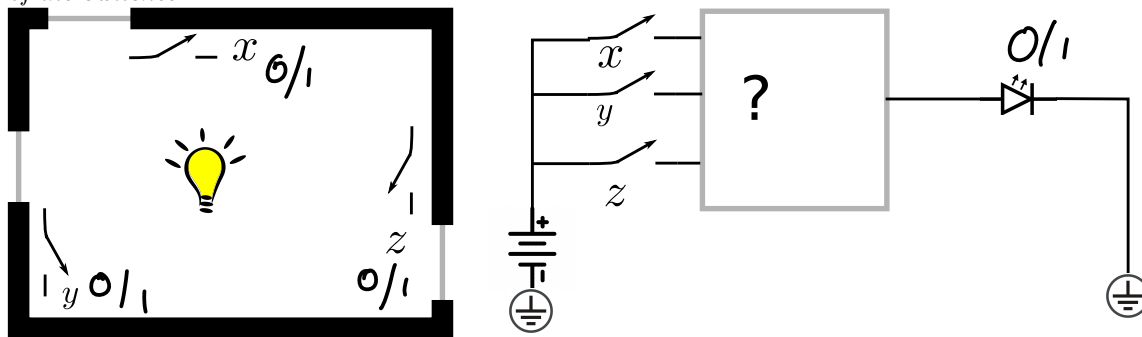Example 1. Assume that a large room has three doors and that a switch near each door controls a light in the room. It has to be possible to turn the light on or off by changing the state of any one of the switches.



Basic Gates


Elementary or the building blocks of digital circuits!

AND Gate




ANSI SYMBOL

Switching circuit

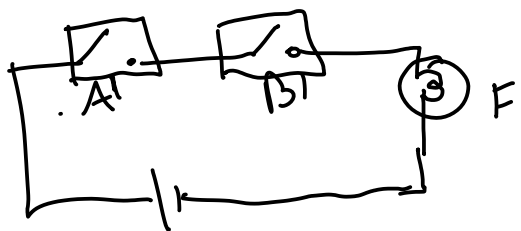

TRUTH TABLE : All possible inputs and corresponding outputs

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

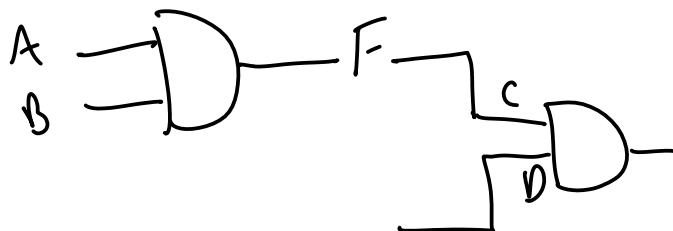

A = Class in Williams T10

B = " on MWF 11-12

A AND B = F : ECE 275 class

① ANSI SYMBOL

② TRUTH TABLE

③ Boolean Algebra notation

$A \cdot B = F$
↑ AND gate


$AB = F$

$F = A \cdot B$


④ VERILOG / SYSTEM VERILOG / C bitwise AND gate

$F = A \& B$

↖ AND gate

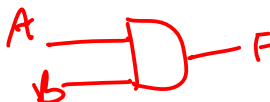



⑤ VENN DIAGRAM

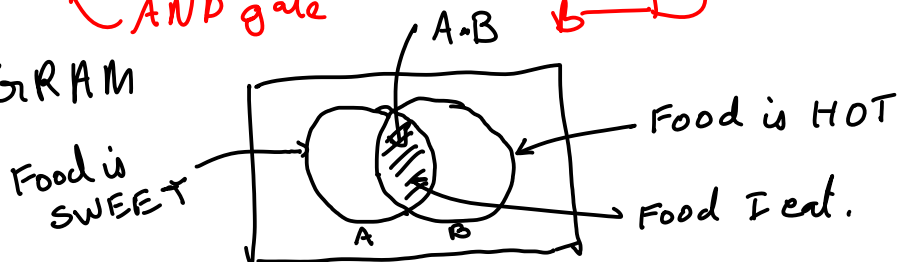

ANSI SYMBOL

0 = FALSE / 1 = TRUE
TRUTH TABLEBoolean
AlgebraC/
VerilogVenn
Diagram



AND

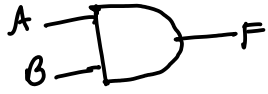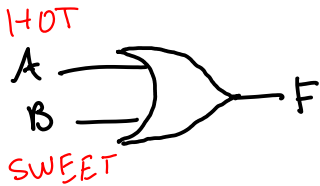OR
gate

	A	B	F
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

$$F = A + B$$


$$F = A | B$$

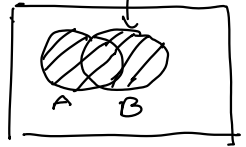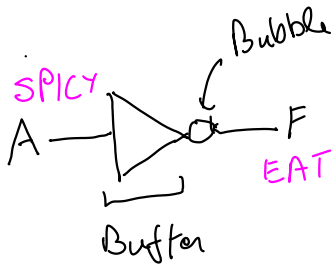NOT
Gate


A	F
0	1
1	0

$$F = \bar{A}$$


$$F = \sim A$$

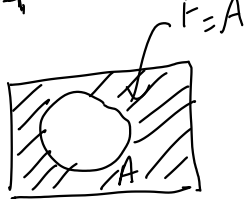

OR Gate Switching circuit

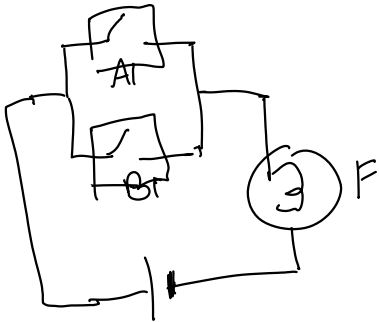

NOT Gate Switching Circuit

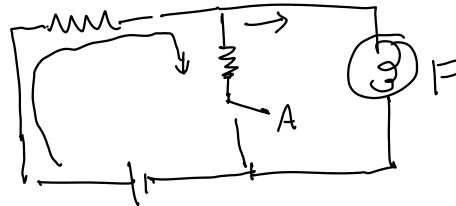


$$F = \bar{A}$$

1.3 Basic Gates and notations summary

Name	C/Verilog	Boolean expr.	Truth Table	Switching circuit	(ANSI) symbol	Venn diagram															
AND Gate	L = x1 & x2	$L = x_1 \cdot x_2$	<table><tr><th>x_1</th><th>x_2</th><th>$x_1 \cdot x_2$</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x_1	x_2	$x_1 \cdot x_2$	0	0	0	0	1	0	1	0	0	1	1	1			
x_1	x_2	$x_1 \cdot x_2$																			
0	0	0																			
0	1	0																			
1	0	0																			
1	1	1																			
OR Gate	L = x1 x2	$L = x_1 + x_2$	<table><tr><th>x_1</th><th>x_2</th><th>$x_1 + x_2$</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x_1	x_2	$x_1 + x_2$	0	0	0	0	1	1	1	0	1	1	1	1			
x_1	x_2	$x_1 + x_2$																			
0	0	0																			
0	1	1																			
1	0	1																			
1	1	1																			
NOT Gate	L = ~ x1	$L = \bar{x}_1 = x'_1$	<table><tr><th>x_1</th><th>\bar{x}_1</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x_1	\bar{x}_1	0	1	1	0												
x_1	\bar{x}_1																				
0	1																				
1	0																				


1.4 Digital circuits or networks

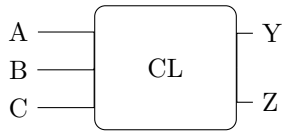

$$Y = F(A, B, C) \quad Z = G(A, B, C)$$

1.5 Two input networks

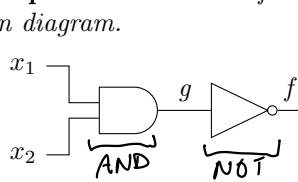
Example 2. Convert the following (ANSI) network into a Boolean expression, a truth table and a Venn diagram.



$g = x_1 \cdot x_2$ (AND)
 $f = \bar{g}$ (NOT)
 $f = \overline{x_1 \cdot x_2}$

x_1	x_2	g	$f = \bar{g}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Venn Diagram

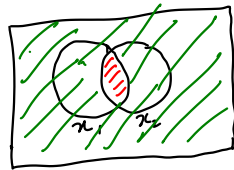


$g = \text{Red}$
 $f = \bar{g}$

Example 3. Convert the following Boolean expression into a (ANSI) network, a truth table and a Venn diagram:

$$f = \overline{x_1 + x_2}$$



Problem 1 (10 marks). Convert the following (ANSI) network into a Boolean expression, a truth table and a Venn diagram.

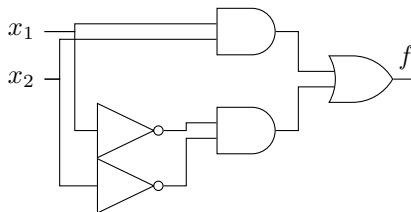

Example 4. Convert the following Boolean expression into a network, a truth table and a Venn diagram:

$$f = x_1\bar{x}_2 + \bar{x}_1x_2$$

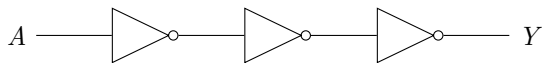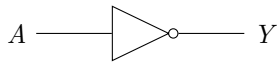
Problem 2 (5 marks). Can two different circuits have the same truth table? Can two different truth tables have the same circuit? Consider the following two circuits for example




Remark 1. Truth tables and Venn diagrams define what the combinational circuit should do. Truth tables define output for every input. Boolean expression and networks define how to achieve the desired input output relationship.

1.6 Multi-input networks

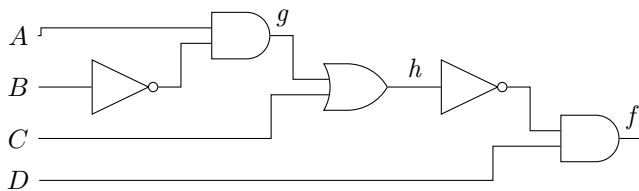Example 5. Convert the following (ANSI) network into a Boolean expression and a truth table.



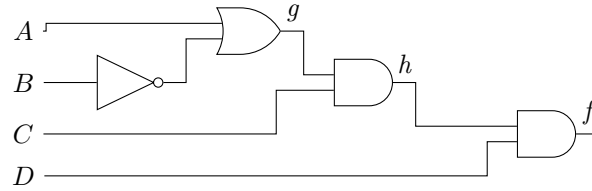Problem 3 (20 marks). Convert the following (ANSI) network into a Boolean expression and a



truth table.

1.7 Minterms and Maxterms

1.7.1 Minterms

Minterm is a product involving all inputs (or complements) to a function. Every row of a truth table has a corresponding minterm. Minterm is true if and only if the corresponding row in the table is active.

Minterms defined as follows for each row of a two input truth table:

A	B	minterm	minterm name
0	0	$\bar{A}\bar{B}$	m_0
0	1	$\bar{A}B$	m_1
1	0	$A\bar{B}$	m_2
1	1	AB	m_3

Consider a two input circuit whose output Y is given by the truth table:

A	B	Y	minterm	minterm name
0	0	0	$\bar{A}\bar{B}$	m_0
0	1	1	$\bar{A}B$	m_1
1	0	0	$A\bar{B}$	m_2
1	1	1	AB	m_3

then $Y = \bar{A}B + AB = m_1 + m_3 = \sum(1, 3)$.

This also gives the *sum of products canonical form*.

Example 6. What is the minterm m_{13} for a 4-input circuit with inputs x, y, z, w (ordered from MSB to LSB).

Problem 4 (5 marks). What is the minterm m_{23} for a 5-input circuit with inputs a, b, c, d, e (ordered from MSB to LSB).

Example 7. Convert the following 4-input truth table into sum of minterms and sum of products canonical form.

minterm name	A	B	C	D	f
m_0	0	0	0	0	0
m_1	0	0	0	1	1
m_2	0	0	1	0	0
m_3	0	0	1	1	0
m_4	0	1	0	0	0
m_5	0	1	0	1	1
m_6	0	1	1	0	0
m_7	0	1	1	1	0
m_8	1	0	0	0	0
m_9	1	0	0	1	0
m_{10}	1	0	1	0	0
m_{11}	1	0	1	1	0
m_{12}	1	1	0	0	0
m_{13}	1	1	0	1	1
m_{14}	1	1	1	0	0
m_{15}	1	1	1	1	0

Problem 5 (10 marks). Convert the following 4-input truth table into sum of minterms and sum of products canonical form.

<i>minterm name</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>f</i>
m_0	0	0	0	0	0
m_1	0	0	0	1	0
m_2	0	0	1	0	0
m_3	0	0	1	1	1
m_4	0	1	0	0	0
m_5	0	1	0	1	0
m_6	0	1	1	0	0
m_7	0	1	1	1	1
m_8	1	0	0	0	0
m_9	1	0	0	1	0
m_{10}	1	0	1	0	0
m_{11}	1	0	1	1	1
m_{12}	1	1	0	0	0
m_{13}	1	1	0	1	1
m_{14}	1	1	1	0	1
m_{15}	1	1	1	1	0

1.7.2 Maxterms

Maxterm is a sum involving all inputs (or complements) to a function. Every row of a truth table has a corresponding maxterm. Minterm is false if and only if the corresponding row in the table is active.

Maxterms are defined as follows for each row of a two input truth table:

<i>A</i>	<i>B</i>	maxterm	maxterm name
0	0	$A + B$	M_0
0	1	$A + \bar{B}$	M_1
1	0	$\bar{A} + B$	M_2
1	1	$\bar{A} + \bar{B}$	M_3

Consider a two input circuit whose output Y is given by the truth table:

<i>A</i>	<i>B</i>	<i>Y</i>	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \bar{B}$	M_1
1	0	0	$\bar{A} + B$	M_2
1	1	1	$\bar{A} + \bar{B}$	M_3

then $Y = (A + B)(\bar{A} + B) = M_0M_2$.

Writing a functional specification in terms of minterms is also called product of sums canonical form.

Example 8. Write the maxterm M_{11} for 4-input Boolean function with the ordered inputs A, B, C, D .

Example 9. Convert the following 4-input truth table into product of maxterms and product of sums canonical form.

<i>maxterm name</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>f</i>
M_0	0	0	0	0	0
M_1	0	0	0	1	0
M_2	0	0	1	0	0
M_3	0	0	1	1	1
M_4	0	1	0	0	0
M_5	0	1	0	1	0
M_6	0	1	1	0	0
M_7	0	1	1	1	1
M_8	1	0	0	0	0
M_9	1	0	0	1	0
M_{10}	1	0	1	0	0
M_{11}	1	0	1	1	1
M_{12}	1	1	0	0	0
M_{13}	1	1	0	1	1
M_{14}	1	1	1	0	1
M_{15}	1	1	1	1	0

Problem 6 (10 marks). Convert the following 4-input truth table into product of maxterms and products of sums canonical form.

<i>maxterm name</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>f</i>
M_0	0	0	0	0	0
M_1	0	0	0	1	1
M_2	0	0	1	0	1
M_3	0	0	1	1	1
M_4	0	1	0	0	1
M_5	0	1	0	1	0
M_6	0	1	1	0	1
M_7	0	1	1	1	1
M_8	1	0	0	0	0
M_9	1	0	0	1	1
M_{10}	1	0	1	0	1
M_{11}	1	0	1	1	1
M_{12}	1	1	0	0	0
M_{13}	1	1	0	1	1
M_{14}	1	1	1	0	1
M_{15}	1	1	1	1	0

Example 10. Write the 3-input truth table for the function $f = m_2 + m_3 + m_7$.

Problem 7 (10 marks). Write the 3-input truth table for the function $f = M_4M_5M_7$.

Problem 8 (10 marks). Write the truth table for the function $f = \bar{A}B\bar{C} + AB\bar{C}$.

Bibliography

- [1] Sarah L Harris and David Harris. *Digital design and computer architecture*. Morgan Kaufmann, 2022.
- [2] Brown Stephen and Vranesic Zvonko. *Fundamentals of digital Logic with Verilog design*. McGraw Hill, 2022.