

Chapter 7

Sequential Logic

7.1 Objectives

1. Understand timing diagrams, gate delays and critical path
2. Design Hazard-free two level circuits
3. Building blocks of sequential circuits
4. Analyze a sequential circuit and derive a state-table and a state-graph
5. Derive a state graph or state table from a word description of the problem
6. Understanding the structure of an FPGA

7.2 Why do we need sequential circuits?


Example 7.1. Think about this problem: Design an occupancy counter that depends on a sensor S at the class door. The sensor is triggered every time a person passes through the door. The counter can be reset to zero with a reset button. Assume we only need up to two bit counter C_1C_0 . Draw a truth table for this circuit. Do you have requisite knowledge for designing this circuit? Can this circuit be designed without a memory element?

state at time t		state/memory		at time $t+1$	
C_1	C_0	S	C_1^+	C_0^+	
0	0	0	0	1	
0	1	0	1	0	
1	0	0	1	1	
1	1	0	0	0	
0	0	1	0	0	
0	1	1	0	1	
1	0	1	0	1	
1	1	1	0	0	

$C_1(t+1) = C_1^+$

7.3 Timing diagrams and propagation delays

 
Example 7.2 (Timing diagram). Draw a timing diagram for an ideal NAND gate.




A — D — Y
B —

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

7.3.1 Delays

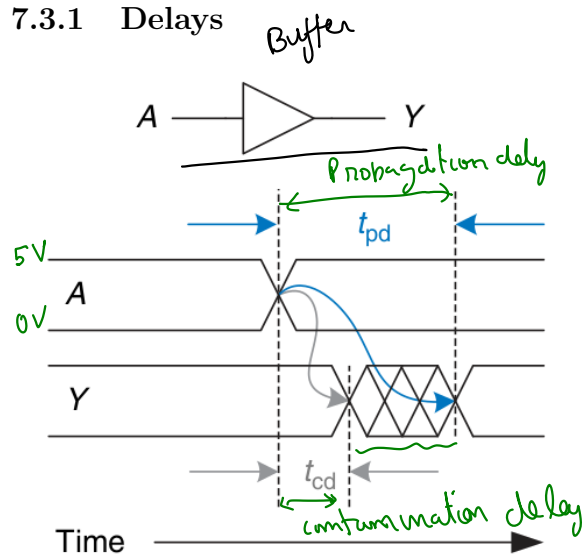

A	Y
0	0
1	1

 


Definition 7.1 (Propagation delay (t_{pd})).

Propagation delay is the time period starting from the change in input to the settling down of the output to a valid steady state.

Definition 7.2 (Contamination delay (t_{cd})).


Contamination delay is the time period from the change in the input to any change in the output.

7.3.2 Paths

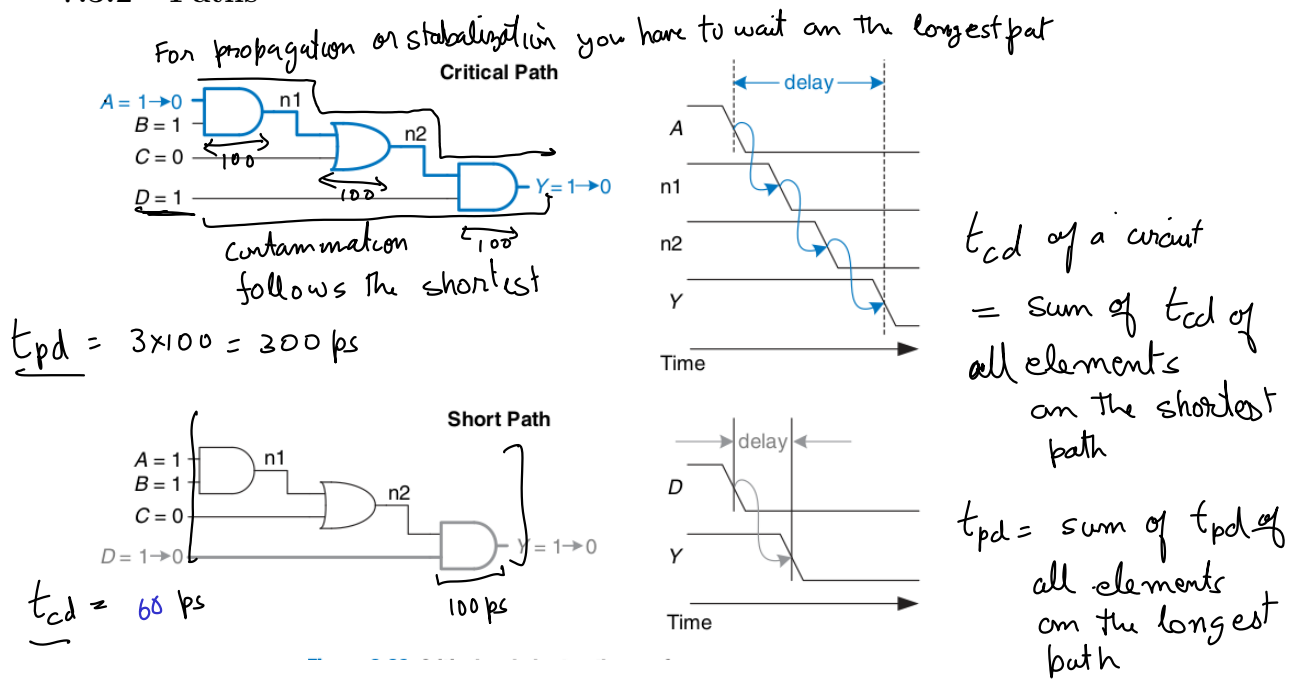

Example 7.3. Find the propagation delay of the circuit above given that propagation delay of each gate is 100ps add contamination delay of 60ps. $t_{pd} = t_{cd}$

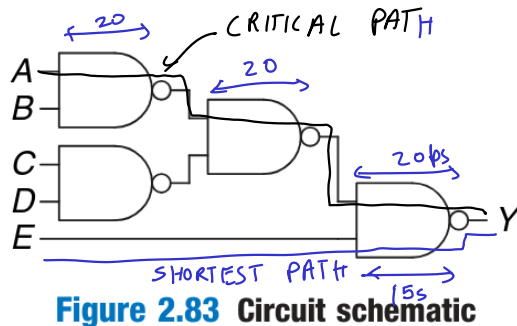Example 7.4 (Ex 2.43 [1]). Determine the propagation delay and contamination delay of the circuit in Figure 7.1. Use the gate delays given in Table 7.2.



$t_{pd} = 60 \text{ ps}$
 $t_{cd} = 15 \text{ ps}$

Table 2.8 Gate delays for Exercises 2.43–2.47

Gate	t_{pd} (ps)	t_{cd} (ps)
NOT	15	10
2-input NAND	20	15
3-input NAND	30	25
2-input NOR	30	25
3-input NOR	45	35
2-input AND	30	25
3-input AND	40	30
2-input OR	40	30
3-input OR	55	45
2-input XOR	60	40

Figure 7.1: Circuit

Table 2.8 Gate delays for Exercises 2.43–2.47

Gate	t_{pd} (ps)	t_{cd} (ps)
NOT	15	10
2-input NAND	20	15
3-input NAND	30	25
2-input NOR	30	25
3-input NOR	45	35
2-input AND	30	25
3-input AND	40	30
2-input OR	40	30
3-input OR	55	45
2-input XOR	60	40

Figure 7.2: Delays

Problem 7.1 (10 marks, Ex 2.44 [1]). Determine the propagation delay and contamination delay of the circuit in Figure 7.3. Use the gate delays given in Figure 7.2.


 


Figure 2.84 Circuit schematic

Figure 7.3: Circuit

7.4 Glitches or Hazards

$$Y = \bar{A}\bar{B} + BC$$

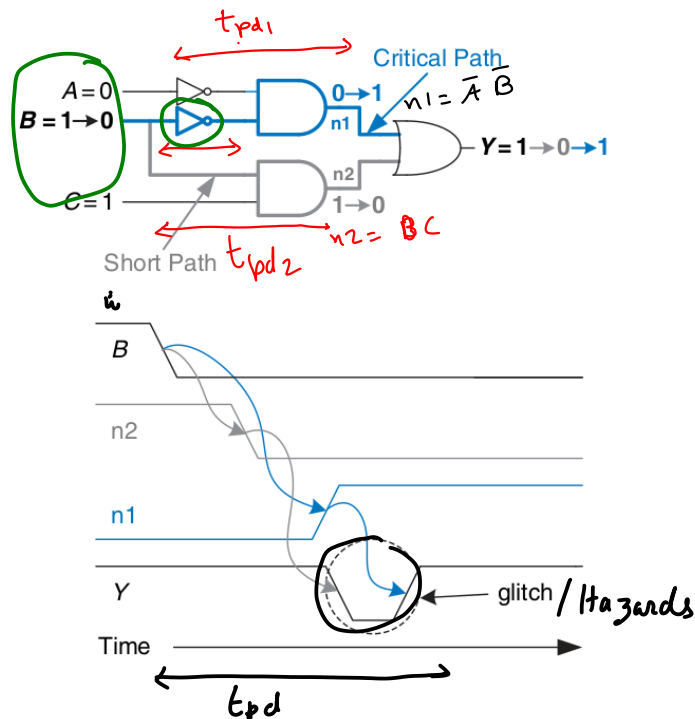

Definition 7.3 (Glitch or Hazard).


Glitch or Hazard is a temporary change in the output of a circuit that is not same as the expected steady state value.

Example 7.5. Design a circuit that fixes the glitch in the above circuit (also known as glitch-free or hazard-free circuit).

$$Y = \bar{A}\bar{B} + BC$$

Hazard free circuit

$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

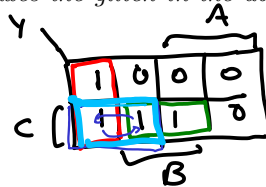






$$A = 0$$

$$C = 1$$

$$B = 1 \rightarrow 0$$


Glitches are caused due transitions between implicants that are adjacent and non-overlapping. Adding an overlapping implicant removes the glitch.

 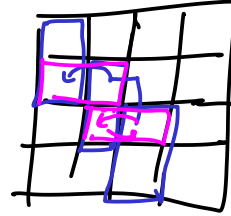 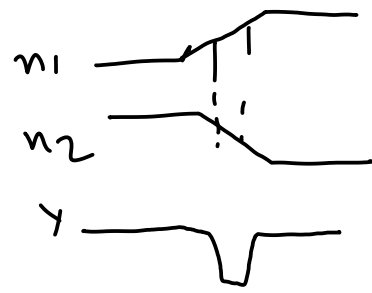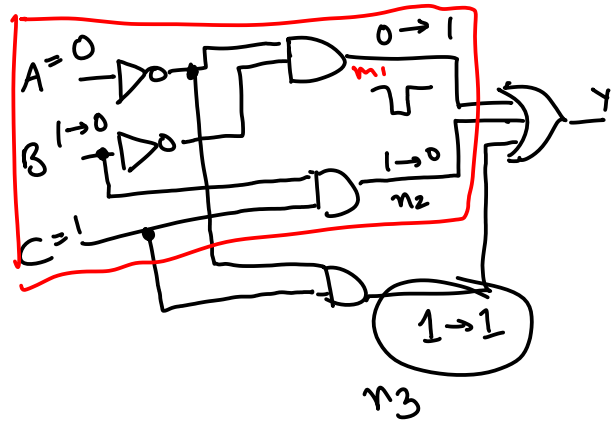Problem 7.2. Find a minimal Boolean equation for the function in Figure 2.85. Remember to take advantage of the don't care entries (marked X) (10 marks).



A	B	C	D	Y
0	0	0	0	X
0	0	0	1	X
0	0	1	0	X
0	0	1	1	0
0	1	0	0	0
0	1	0	1	X
0	1	1	0	0
0	1	1	1	X
1	0	0	0	1
1	0	0	1	0
1	0	1	0	X
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	X
1	1	1	1	1

Figure 2.85 Truth table for Exercise 2.28

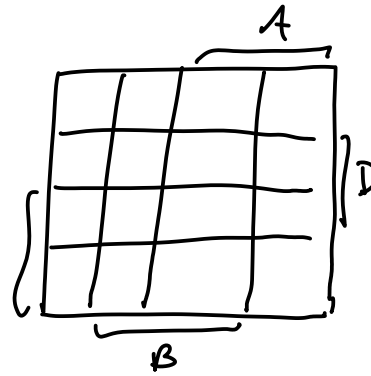


1. Sketch a circuit for the function (10 marks).
2. Does your circuit from have any potential glitches when one of the inputs changes? If not, explain why not. If so, show how to modify the circuit to eliminate the glitches (10 marks).

7.5 How to create memory element from circuits

Two types of memory

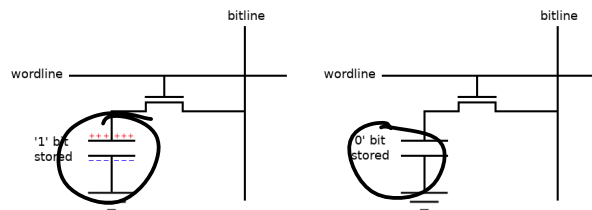1. Volatile memory. For example, RAM, CPU registers.
2. Non-volatile memory. For example, SSD, Flash drives. (Not covered in this course)
 - (a) Memories that require periodic refreshing. For example, DRAM: Dynamics Random Access memory (Not covered in this course)



1

- (b) Memories that are always refreshing. For example, SRAM: Static Random Access memory [3, Appendix B.64]


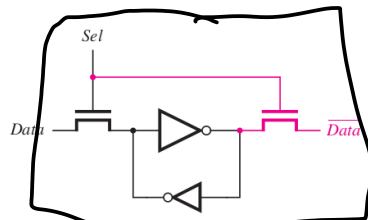


Figure B.64 An SRAM cell.

¹Image source: allaboutcircuits.com/technical-articles/introduction-to-dram-dynamic-random-access-memory/

7.6 Latches and Flip-Flops [1, Sec 3.2]

Example 7.6 (Ring oscillator). [1, Sec 3.31] How many stable states does the following circuit have?

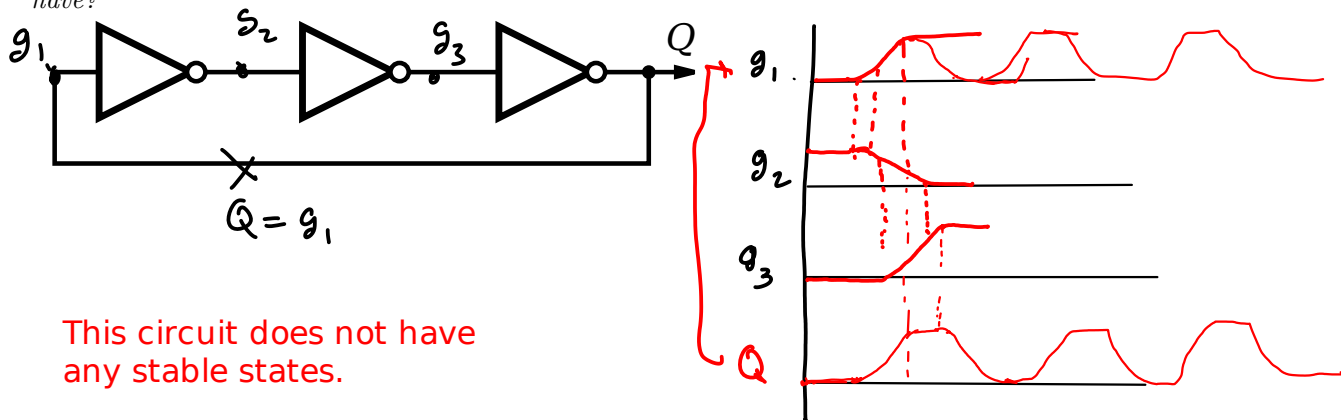

Definition 7.4 (Astable circuits).

Circuits without a stable state are called astable circuits.

Example 7.7. Analyze the timing diagram of the following circuit.

 
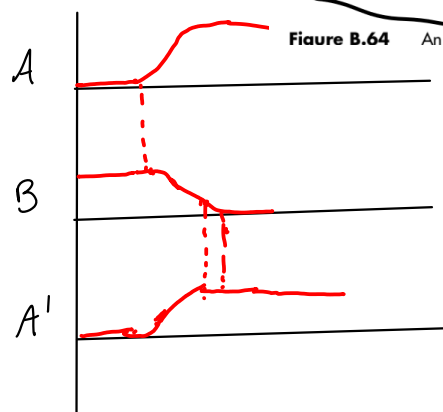
 




Figure B.64 An SRAM cell.

A stable state is a state of circuit, when the circuit stays in that state if initialized into that.

Definition 7.5 (Bistable circuits).


Bistable circuits have two stable states

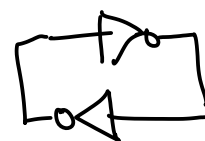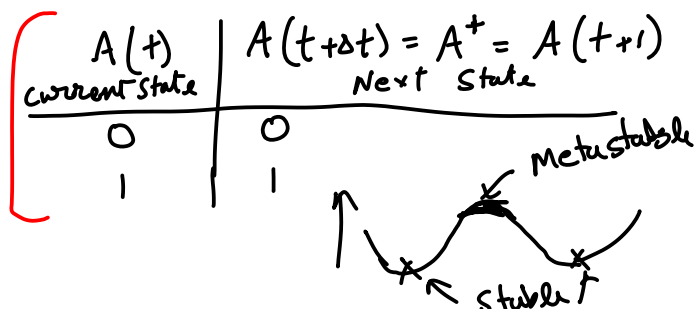Definition 7.6 (Characteristic or state table). Draw the characteristic or state table of the above circuit.



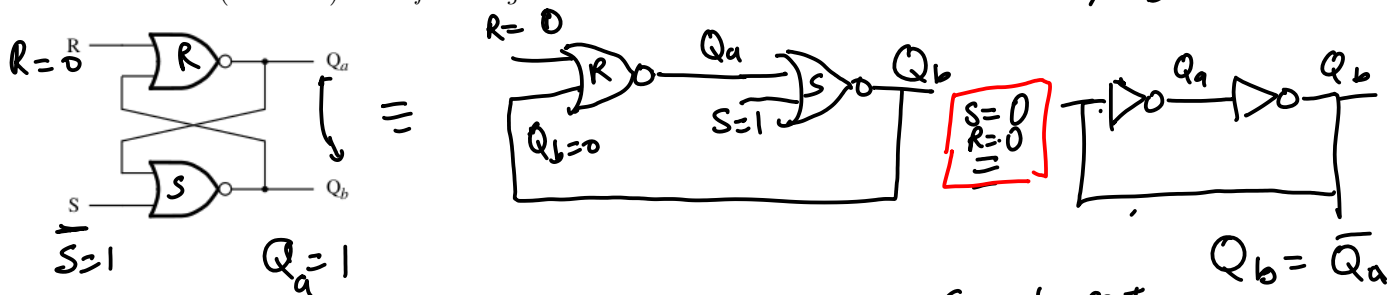
7.6.1 SR (Set-Reset) latch [1, Sec 3.2.1]

Definition 7.7 (SR latch). The following circuit is called the SR latch.




1. How many stable states does this circuit have?
2. Draw its characteristic or state table.
3. Draw SR latch symbol

S	R	Q_a	Q_a^+	
0	0	0	0	Hold
0	0	1	1	
0	1	0	0	Reset
0	1	1	0	
1	0	0	1	Set
1	0	1	1	
1	1	0	x	undefined/indeterminate
1	1	1	x	

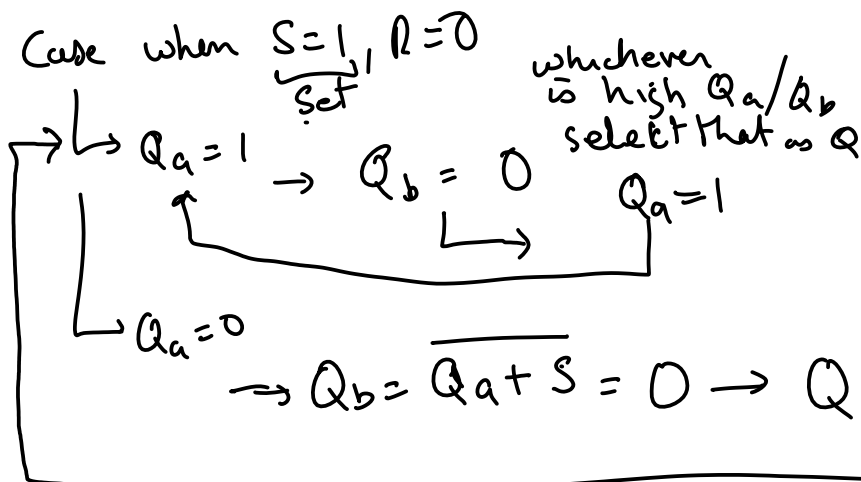

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

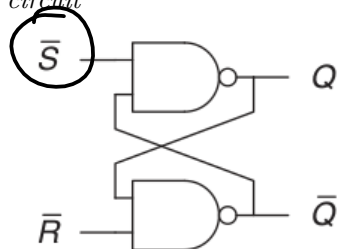Problem 7.3 (SR latch using NAND gates). Draw the characteristic or state table for the following circuit



when $S=0, R=1$
Reset

$$\rightarrow Q_a = 1$$


$$Q_b = \overline{Q_a + S} = 0$$

$$Q_a = \overline{Q_b + R} = 0$$

$$\rightarrow Q_a = 0$$

$$Q_b = \overline{Q_a + S} = 1$$

$$Q_a = \overline{Q_b + R} = 0$$


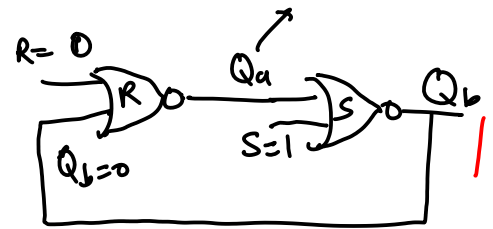


A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

S	R	Q^+
0	0	Q } Hold
0	1	0 } Reset
1	0	1 } Set
1	1	X

 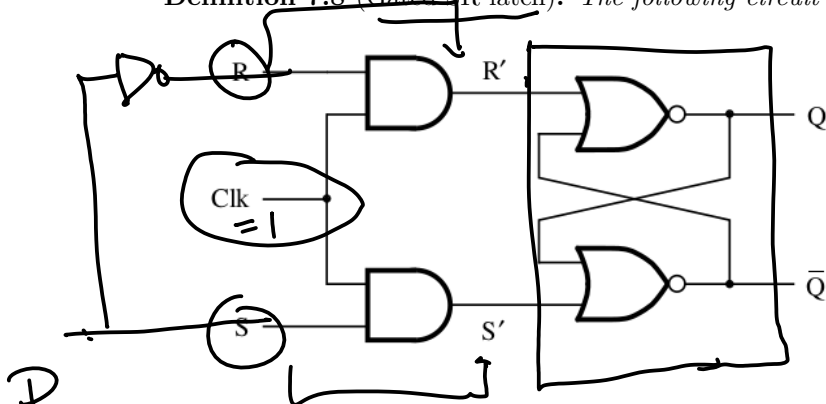7.6.2 Gated SR latch [3, Sec 5.2]


Definition 7.8 (Gated SR latch). The following circuit is called the Gated SR latch.



clk	R	R'
0	0	0
0	1	0
1	0	0
1	1	1

1. Draw its characteristic table.

2. Draw the Gated SR latch symbol

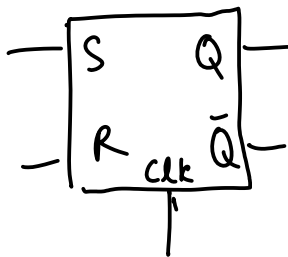

clk	S	R	Q ⁺
0	*	*	Q
1	0	0	Q
1	0	1	0
1	1	0	1
1	1	1	X

Hold
Reset
Set
indeterminate state



clk	R'
0	0
1	R

A clock input to the latch makes the state affected by input only when the clock is high.

Latches are level triggered (opposite to edge-triggered as in flip flops)

  7.6.3 D (Data) latch [1, Sec 3.2.2] Transparent latch

Definition 7.9 (D latch). The following circuit is called the D latch.




clk	D	Q ⁺
1	0	0
1	1	1
0	*	Q
0	*	Q

1. Draw its characteristic table.

2. Draw the D latch symbol

clk	Q ⁺
0	Q
1	D

 

Problem 7.4. Consider the timing diagram in Figure 7.4. Assuming that the D and Clock inputs shown are applied to the circuit in Figure 7.5, draw waveforms for the Q_a , Q_b , and Q_c signals. (10 marks) [?, Prob 5.1]


 
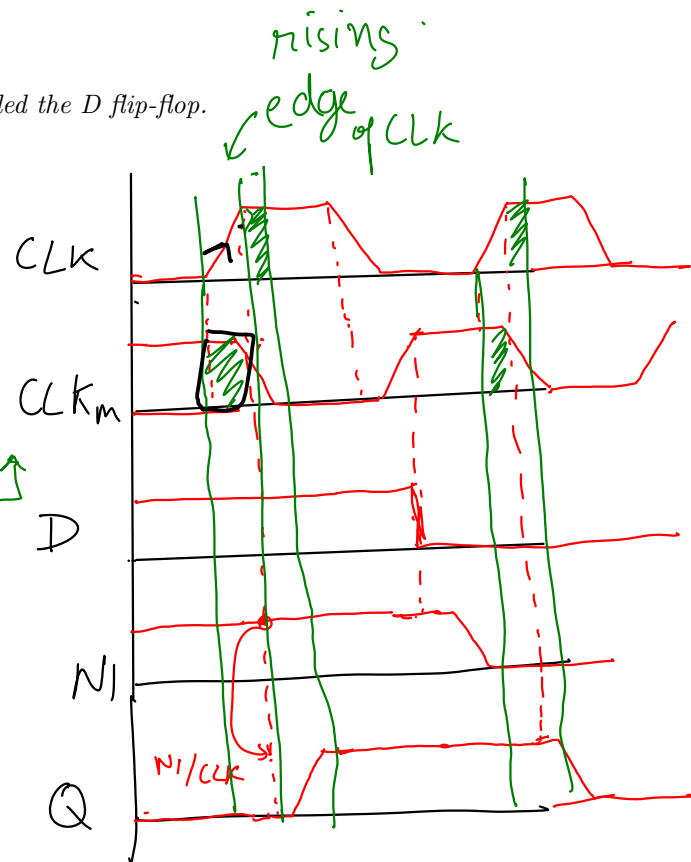




Figure 7.4: Inputs for Prob 7.4

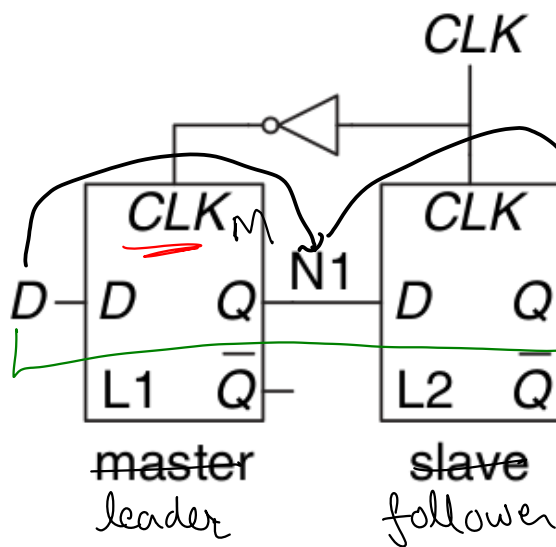7.6.4 D flip-flop [1, Sec 3.2.2]


Definition 7.10 (D flip-flop). The following circuit is called the D flip-flop.



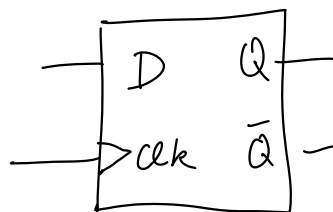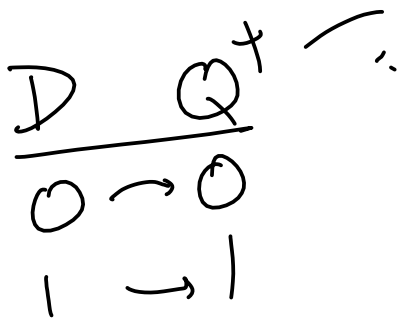1. Draw its timing diagram
2. Draw its characteristic table.
3. Draw the D flip-flop symbol



clk	D	Q ⁺
↑	0	0
↑	1	1
★	★	Q

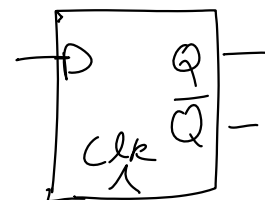

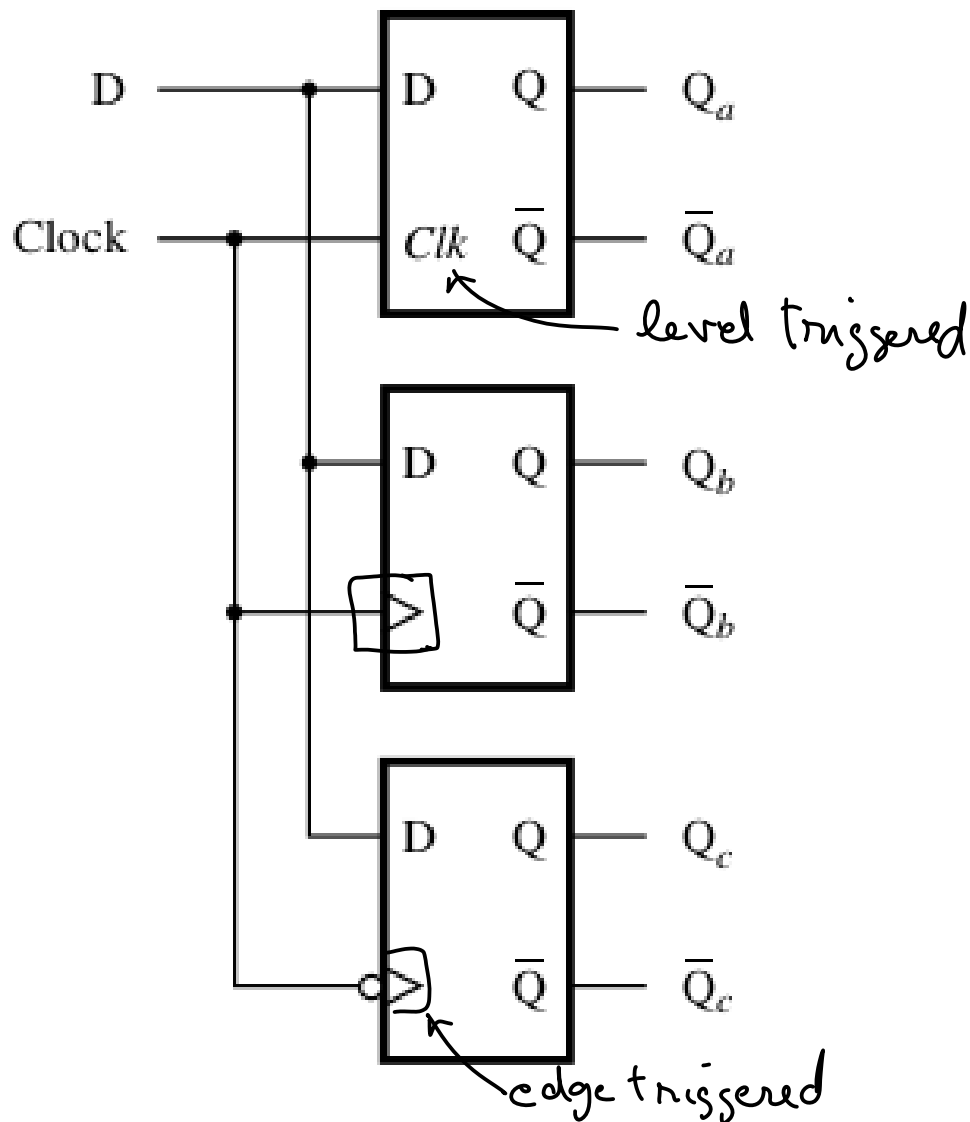





Figure 7.5: Circuit for Prob 7.4. Recall that Clk with a “▷” symbol indicates rising-edge (positive-edge) triggered flip-flop. Clk without “▷” symbol indicates a level-triggered latch. Clk with “◁” symbol indicates a falling-edge (negative-edge) triggered flip-flop.

Remark 7.1. What is the difference between a latch and a flip-flop?

Latches are level-triggered: The states gets affected from inputs when clock is high

Flip-flops are edge-triggered: The states get affected from inputs at the rising edge of the clock

 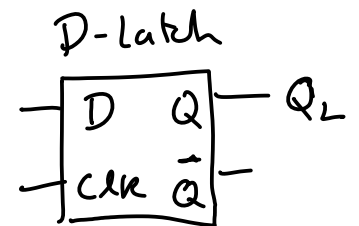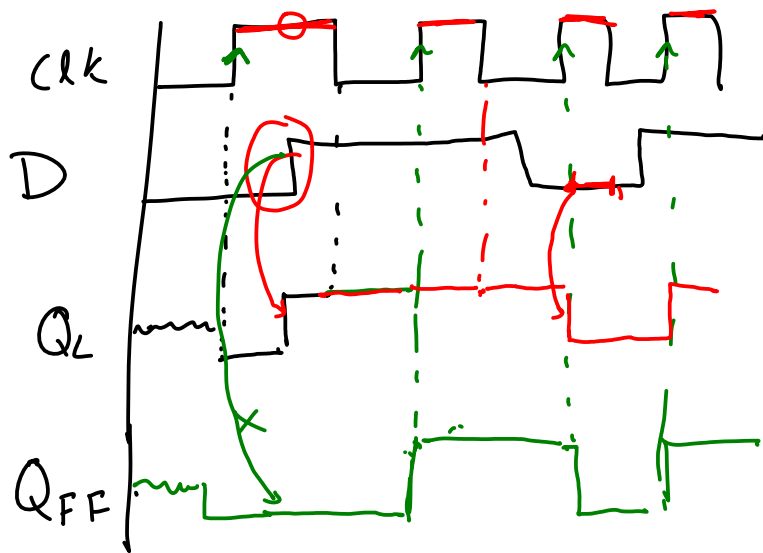Example 7.8. Add a RESET signal to the D flip-flop that resets the state of flip-flop to 0.





D-ff

Asynchronous sequential circuits: not synchronized with the clock. E.g. Latches.

Synchronous sequential circuits: circuits synchronized with the clock. All states and outputs change at the rising edge of the clock. E.g. Flip flops, combinations circuits

You want to stick with Synchronous sequential circuits.

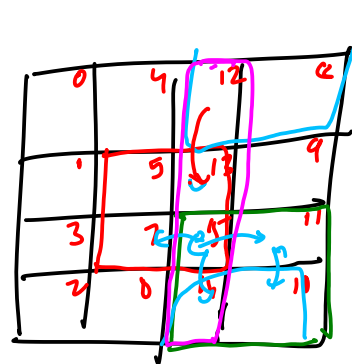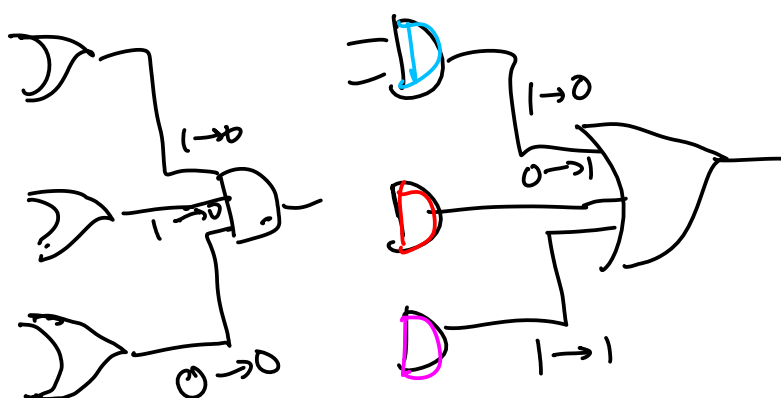1. No loops in the circuit without a flip flop. If there is a loop then there is a flip flop on that loop.
2. The propagation delay in the loop should be smaller than the clock cycle.



Synchronous vs Asynchronous sequential circuits


Latches X

Flip flop ✓

edge-triggered

optional (Mealy)

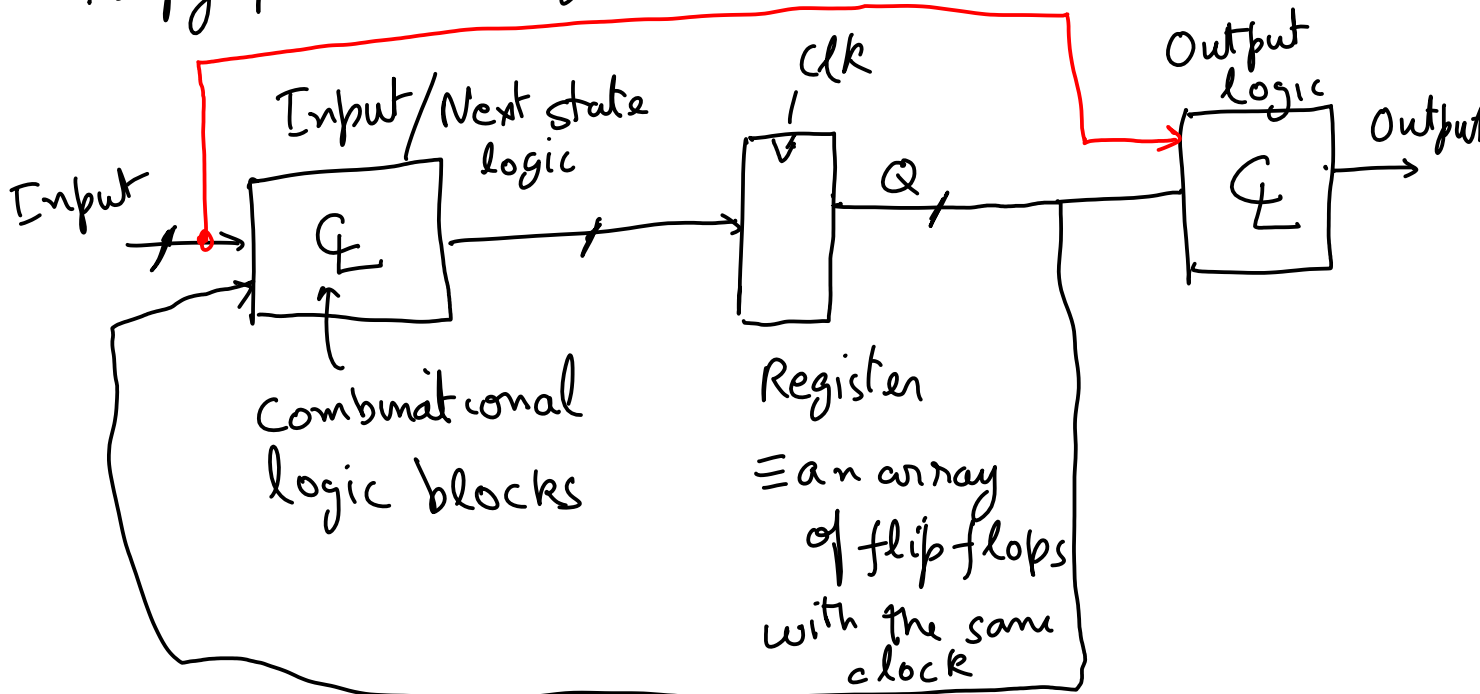MOORE if the optional connection is not used



① D-fl (Data/Delay) ② T-fl (Toggle) ③ J-K fl (Set/Reset)

Example 7.9. The toggle (T) flip-flop has one input, CLK, and one output, Q. On each rising edge of CLK, Q toggles to the complement of its previous value. Draw a schematic for a T flip-flop using a D flip-flop and an inverter.

D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1

D	Q ⁺
0	0
1	1

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

Hold (for T=0), Toggle (for T=1)

T	Q ⁺
0	Q
1	\overline{Q}

Set	Reset	Q ⁺	
J	K		
0	0	Q	Hold
0	1	0	Reset
1	0	1	Set
1	1	\overline{Q}	Toggle

Problem 7.5. A JK flip-flop receives a clock and two inputs, J and K. On the rising edge of the clock, it updates the output, Q. If J and K are both 0, Q retains its old value. If only J is 1, Q becomes 1. If only K is 1, Q becomes 0. If both J and K are 1, Q becomes the opposite of its present state.


- Construct a JK flip-flop using a D flip-flop and some combinational logic.
- Construct a D flip-flop using a JK flip-flop and some combinational logic.
- Construct a T flip-flop (see Exercise 3.9) using a JK flip-flop.

7.7 Finite State Machines [1, Sec 3.4]

2

Example 7.10. Design an occupancy counter that depends on a sensor S at the class door. The sensor is triggered every time a person passes through the door. Assume that the counter starts at zero. Assume we only need up to two bit counter C₁C₀. Draw a state table for this circuit.

 Problem 7.6. A divide-by-N counter has one output and no inputs. The output Y is HIGH for one clock cycle out of every N. In other words, the output divides the frequency of the clock by N. The waveform for a divide-by-3 counter is shown here:



Sketch circuit designs for such a counter

²These notes will not fit on your note sheet.

D	$Q^+ \leftarrow \text{next state}$
0	0
1	1

D-fl

T	$Q^+ \leftarrow \text{next state}$
0	$Q \leftarrow \text{prev state}$
1	\bar{Q}

Toggle-fl

Set	Reset	Q^+
J	K	
0	0	Q Hold
0	1	0 Reset
1	0	1 Set
1	1	\bar{Q} Toggle

Sequential logic circuit

Synchronous




Finite state machines

$k\text{-ff} \Leftrightarrow 2^k \text{ states}$

Turing machines

Moore \rightarrow Output only depends on current state

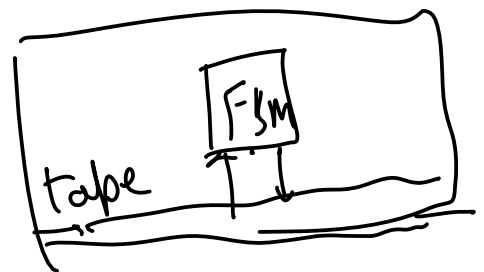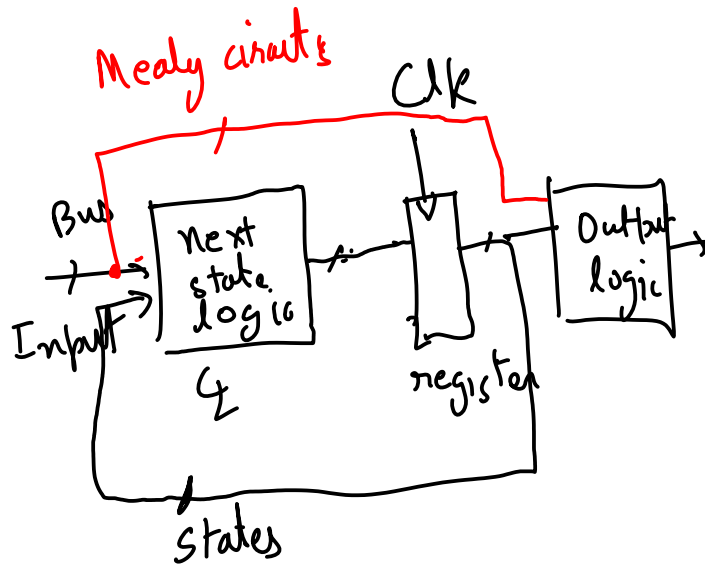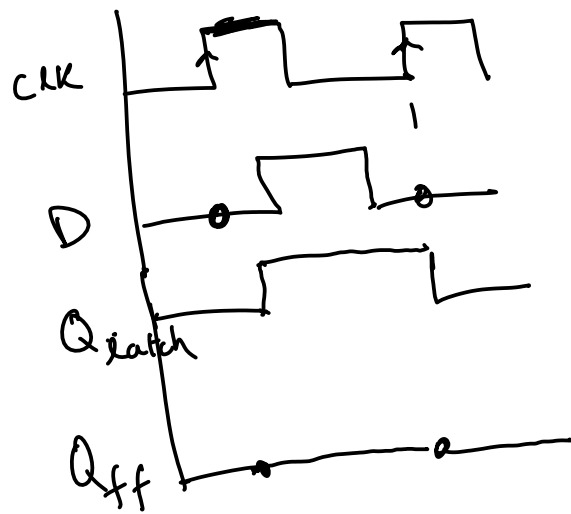Mealy \rightarrow Output depends on current state and current input




Design a D-ff from JK-ff

$$J = D$$

$$K = \overline{D}$$

D	Q	J	K
0	0	0	d
0	1	d	d
1	0	d	0
1	1	d	0

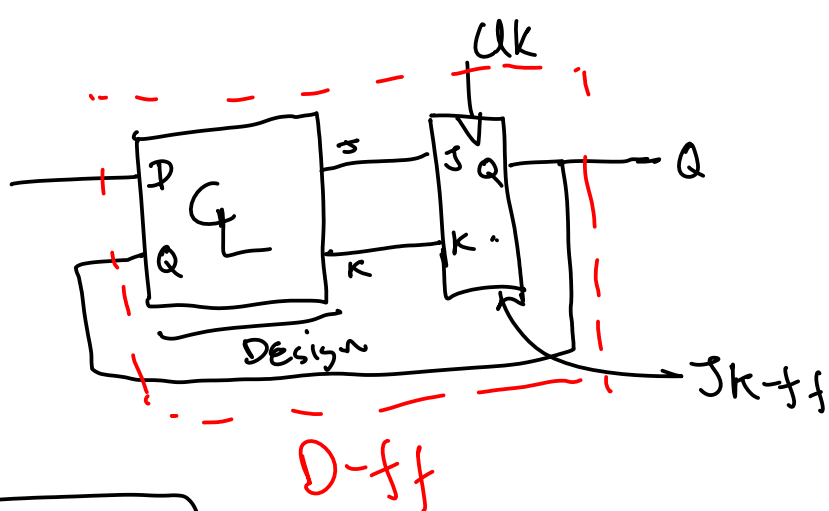



D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1

	Q → Q ⁺	J	K
Reset/Hold	0 → 0	0	$\overline{0} \rightarrow d$
Set/Reset	0 → 1	1	d
Reset/Reset	1 → 0	d	1
Set/Hold	1 → 1	d	0

Excitation Table

J	K	Q ⁺
0	0	Q
0	1	0
1	0	1
1	1	\overline{Q}

  What ff inputs will give you a desired "excitation" that is Q → Q⁺ transition.




Design a T-ff using a D-ff

want

\overline{T}	Q	D
0	0	0
0	1	1
1	0	1
1	1	0

$$D = T \oplus Q$$

$$= \overline{T}Q + T\overline{Q}$$

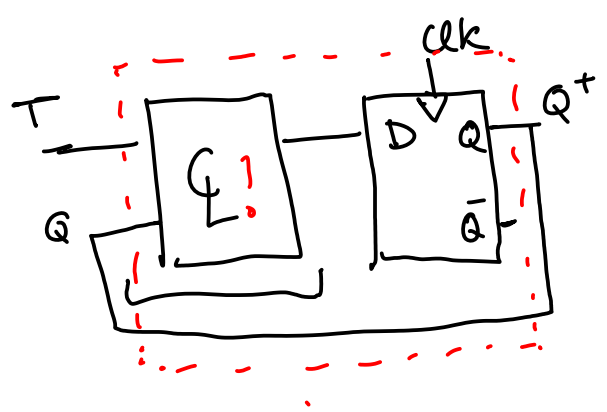

I have characteristic table of T-ff


T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

and Excitation table of D-ff

Q^x	Q^+	D
0	0	0
0	1	1
1	0	0
1	1	1

D	Q^x	Q^+
0	0	0
0	1	1
1	0	0
1	1	1

Desired
state
transition
table

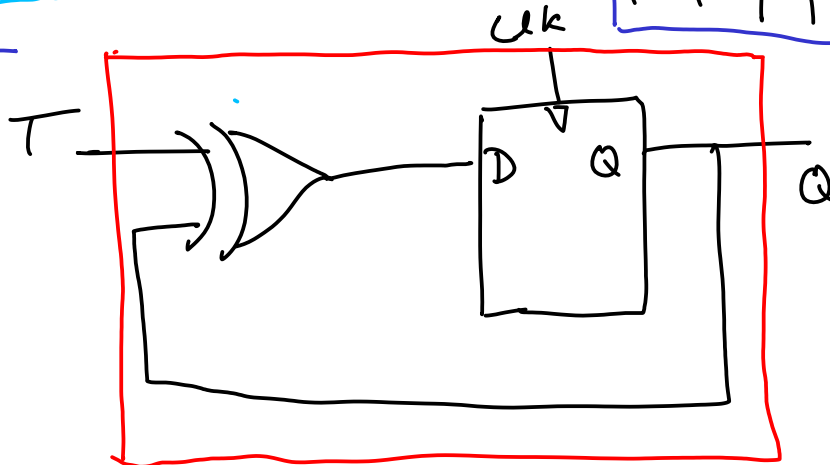

1. Decided on a ff, draw a block diagram to convert sequential circuit design to combinational logic design
2. We want to find the truth table for the combinational logic design
3. Write down the desired state transition table and the excitation table of the flip flop used.
4. Combine both to get the the truth table for combinational logic.


Design a D-ff using a T-ff

Design a D-flip using a T-flip

Want

D	Q	T
0	0	0
0	1	1
1	0	1
1	1	0

$$T = D \oplus Q$$

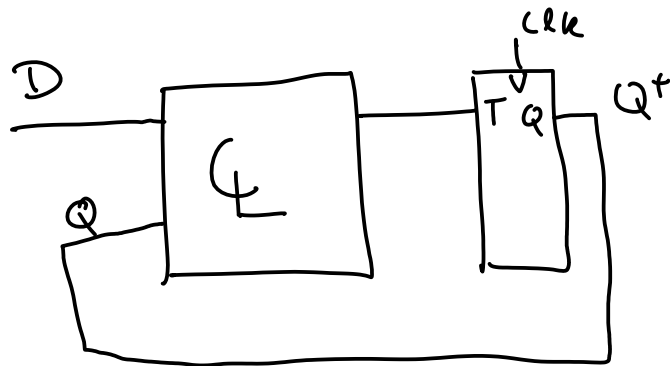

State transition table

D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1

Excitation table

For each possible state transition, what should the input to my flip flop be?

Q	Q ⁺	T
0	0	0
0	1	1
1	0	1
1	1	0

Excitation table for J-K ff

Q	Q ⁺	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

Hold/Reset

Toggle/Set

Toggle/Reset

Hold/Set

J	K	Q ⁺
0	0	Q
0	1	0
1	0	1
1	1	\overline{Q}

if $S=0$

$C_1 C_0 = C_1 C_0$


if $S=1$

$C_1 C_0 = C_1 C_0 + 1$

numerical addition

next states

S	Prev states		next states	
	C_1	C_0	C_1^+	C_0^+
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0

 

States $C_1 C_0$
2-bits
of memory

D	Q^+
0	0
1	1

$Q^+ = D$

D_1

C_0	S			
	0	1	1	0
0	0	1	1	0
1	0	1	0	1

C_1


$D_1 = C_1 \bar{C}_0 + \bar{S} C_1 + S \bar{C}_1 C_0$

D_0

C_0	S			
	0	0	1	1
0	1	1	0	0
1	1	1	0	0



C_1

$D_0 = S \bar{C}_0 + \bar{S} C_0$

 

How many states? $\text{ceil}(\log_2(3)) = 2$

$$2^1 < 3 \leq 2^2$$

  


Problem 7.7. Design a 3-bit counter which counts in the sequence: 001, 011, 010, 110, 111, 100, (repeat) 001, ...

Example 7.11. Design an odd-even counter for an single bit input. The output of this circuit should be 1 if the number of 1s to the input have been odd so far and 0 otherwise.

Example 7.12 (Sequence detectors). A sequential circuit has one input and one output. The output becomes 1 and remain 1 thereafter when at least two 0's and at least two 1's have occurred as inputs regardless of the order of

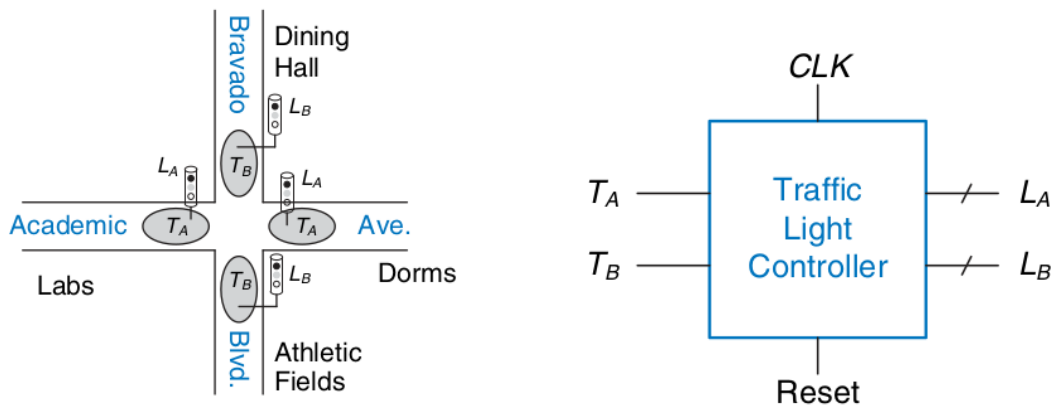
Example 7.13. Consider the problem of inventing a controller for a traffic light at a busy intersection on campus. There are two traffic sensors, T_A and T_B , on Academic Ave. and Bravado Blvd., respectively. Each sensor indicates TRUE if students are present and FALSE if the street is empty. There are two traffic lights, L_A and L_B , to control traffic. Each light receives digital inputs specifying whether it should be green, yellow, or red. When the system is reset, the lights are green on Academic Ave. and red on Bravado Blvd. As long as traffic is present on Academic Ave., the lights do not change. When there is no longer traffic on Academic Ave., the light on Academic Ave. becomes yellow for 5 seconds before it turns red and Bravado Blvd.'s light turns green. Similarly, the Bravado Blvd. light remains green as long as traffic is present on the boulevard, then turns yellow and eventually red.



1. Draw a state transition diagram
2. Draw a state table
3. Assign binary encodings to each of the states
4. Redraw the state table with binary encodings. Design a minimal SOP boolean expression.
5. Assign binary encodings to each of the output and redraw the output table. Design a minimal SOP boolean expression for the outputs.

Problem 7.8. Design a circuit for a 2×2 pixel resolution pong game, where the ball can only occupy 4 possible pixels and a single paddle occupies another 2 pixels. The ball bounces off the paddle when the paddle is in the correct row. To keep it interesting, the ball takes a different path from the source path. Track the score with a single bit counter.

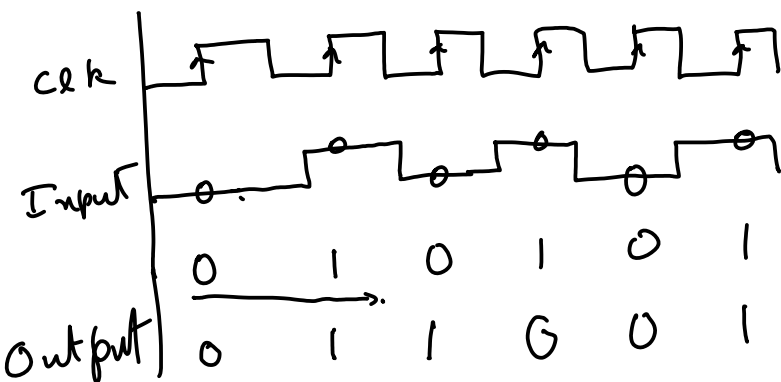Example 7.11. Design an odd-even counter for an single bit input. The output of this circuit should be 1 if the number of 1s to the input have been odd so far and 0 otherwise.




Example

Input: 0 1 1 1 0 1 0 1 0 1 0
 Output: 0 1 0 1 1 0 0 1 1 0 0

Is it sequential or combinational? Yes

How much memory? How many states does this circuit need? = 2 states = 1-bit memory = 1-ff

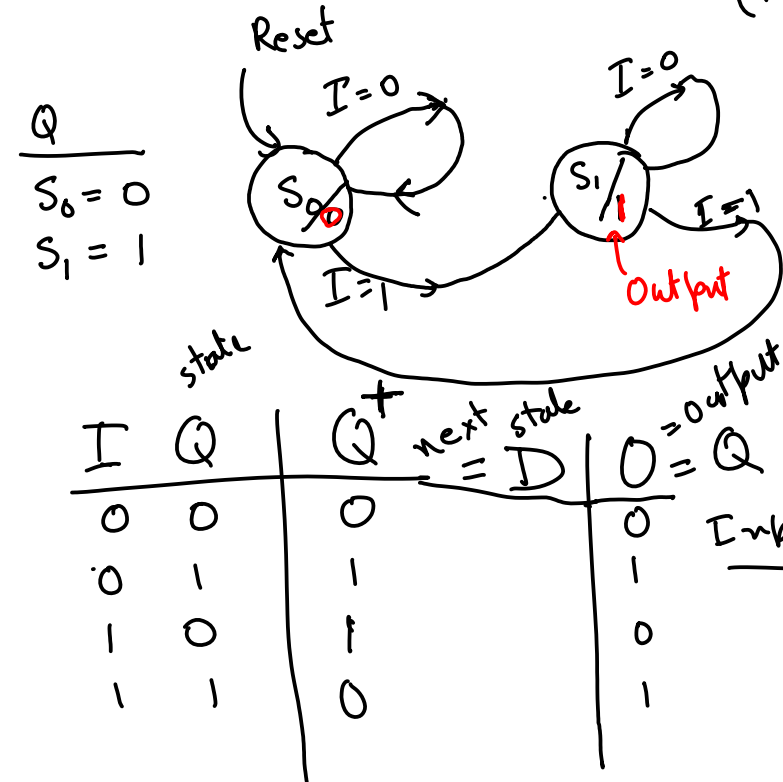
State diagram/State transition diagram (Moore)



State assignment (guideline methods)

S_0	0 0 ?
S_1	1 1 ?
S_2	1 1 ?
S_3	
S_4	
S_5	


I	Q	Q ⁺ next state = D	Q = output
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	1

 

Next state table/State transition table/State table


I	Q	D	Truth table
0	0	0	
0	1	1	
1	0	1	
1	1	0	

$$D = I \oplus Q$$

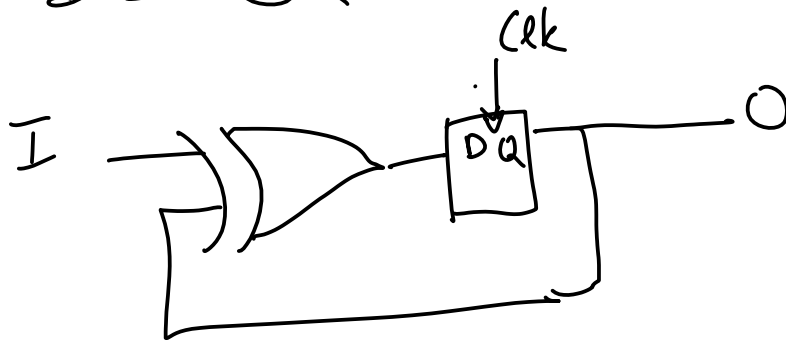


 Example 7.12 (Sequence detectors). A sequential circuit has one input and one output. The output becomes 1 and remains 1 thereafter when at least two 0's and at least two 1's have occurred as inputs regardless of their order of

Input 0 1 1 1 0 1 0 1 0 1 0
 Output 0 0 0 0 1 1 1 1 1 1 1
 Reset



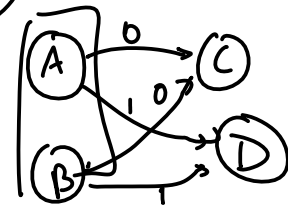Try to reuse the same states as much as possible. If two states have the same next states and outputs for corresponding inputs, then the two states are equivalent.



- 0 S_0 = Haven't seen any 0s or 1s
- 1 S_1 = seen 1 zero
- 2 S_2 = seen 1 one
- 3 S_3 = seen 2 zeros = seen at least 2 zeros

4 S_4 = seen 1 zero / 1 one
 5 S_5 = seen 1 zero / 1 one
 Merged


- 6 S_6 = seen 2 ones = seen at least 2 ones
- 7 S_7 = at least 2 zeros + seen 1-one
- 8 S_8 = at least 2 ones + seen 1-zero
- 9 S_9 = at least 2 zeros + seen 2 ones

9 states = ff?

State reduction techniques and algorithms

- Row reduction
- Implication tables

Guideline method
Register

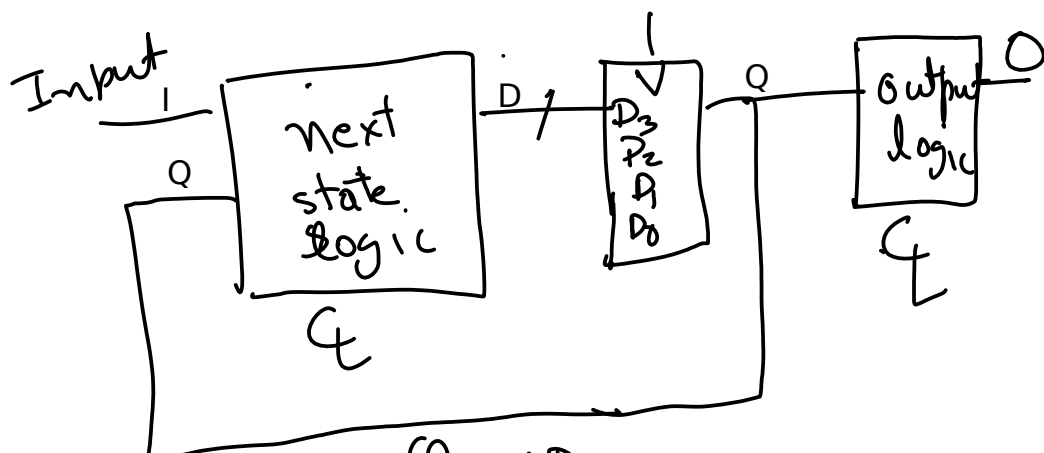


	D_3	D_2	D_1	$Q_{3:0}$	D_0
I	Q_3^+	Q_2^+	Q_1^+	Q_0^+	$O(Q_{3:0})$

March 28,


Finite state machines

1. Moore: the output depends only on the state
2. Mealy: the output depends on both state and the input

 Example 7.12 (Sequence detectors). A sequential circuit has one input and one output. The output becomes 1 and remain 1 thereafter when at least two 0's and at least two 1's have occurred as inputs regardless of the order of



State transition diagram

 

$S_0 = 0-0$

$S_1 = 1-0$

$S_2 = 0-1$

$S_3 = 2-0$


$S_4 = 1-1$

$S_5 = 0-2$

$S_6 = 2-1$

$S_7 = 1-2$

$S_8 = 2-2$

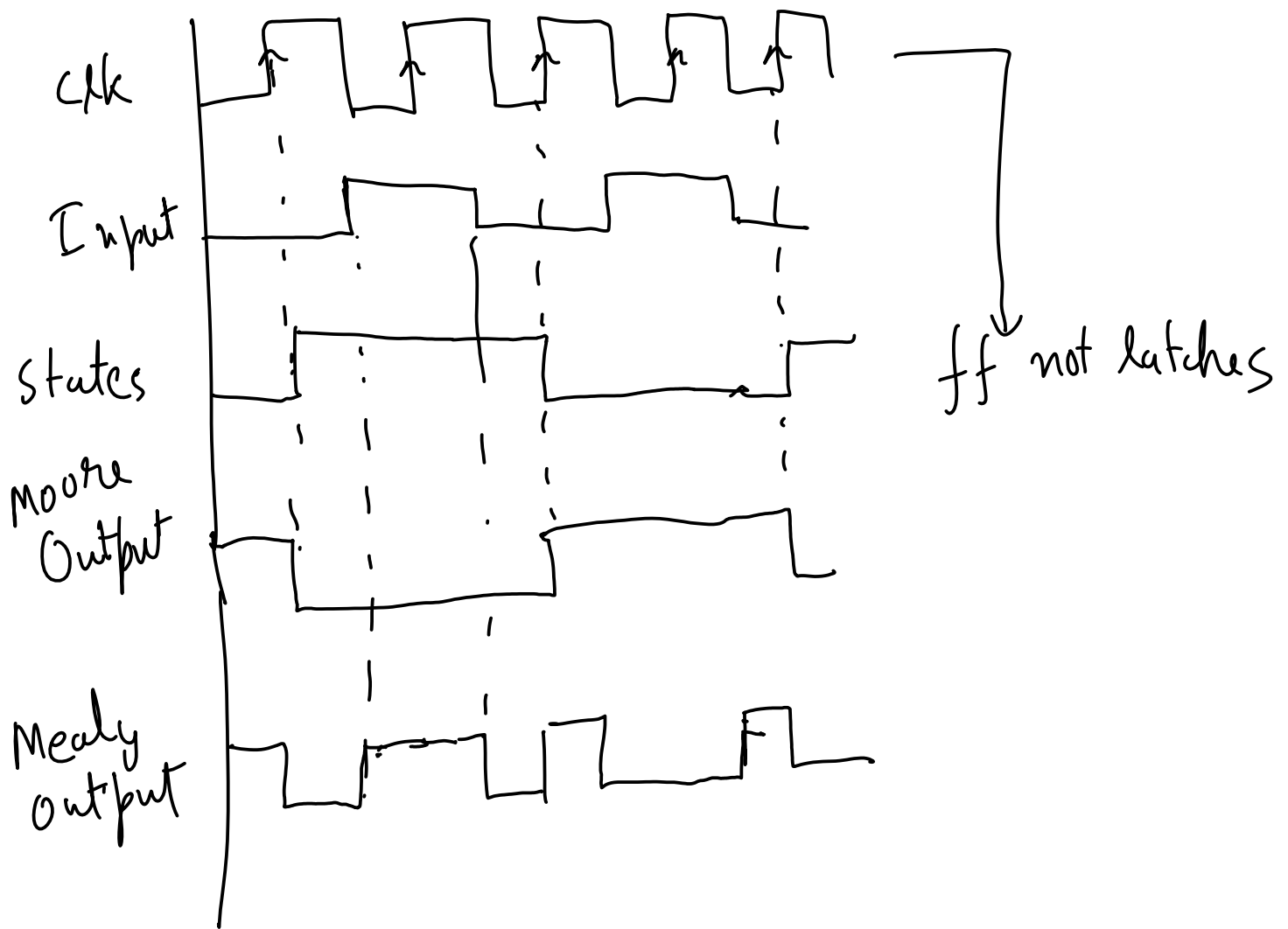

Advantages and disadvantages:

1. Moore: Makes the input synchronized with the clock/ Mealy: causes the output to vary with input
2. Moore: Needs more (or equal) states than a Mealy design.

Your circuit has one input and one output. Detect a sequence 0101 or 0110. Whenever the sequence is detected, the system does not reset and outputs a 1 for one clock cycle.


Example:

Input: 0 0 0 1 0 1 1 0 0 1 1 0 1

Output: 0 0 0 0 0 1 0 1 0 0 0 1 0

MOORE

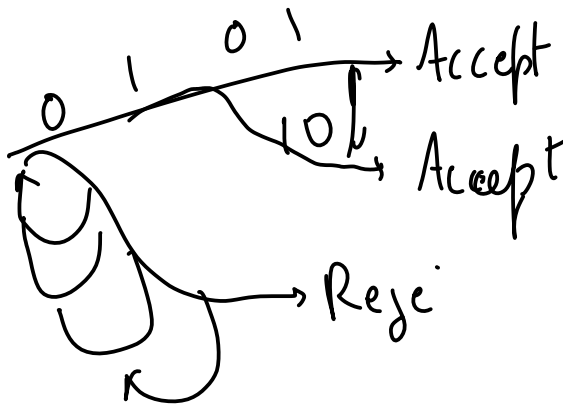Draw Moore state transition diagram for this problem



Acceptable sequences seen so far

$S_0 = **$
 $S_1 = *0$
 $S_2 = **01$
 $S_3 = *010$
 $S_4 = *011$
 $S_5 = 0101$
 $S_6 = 0110$