
 


Chapter 6

Muxes and Decoders

Sometimes building blocks of circuit can be larger than simple gates. Having larger building blocks reduces the number of inter-connection switches.

PLA

 


6.1 Objectives

1. Design combinational circuits using multiplexers and decoders

6.2 Design combinational circuit using multiplexers [1, Section 2.8.1]



6.2.1 Review: 2to1 Multiplexer (MUX)

 

S	Y
0	D_0
1	D_1

S_0	D_1	P_2	Y
0	0	0	0
0	0	1	0
:	:	:	:
1	1	1	1

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

  


$$Y = S D_1 + \bar{S} D_0$$

$$Y = D_0 \bar{S} + D_1 S$$

 6.2.2 Wider multiplexers

Draw the symbol for a 4:1 MUX, an 8:1 MUX and a $2^N : 1$ MUX and write corresponding Boolean expressions.




S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$Y = \underbrace{\bar{S}_1 \bar{S}_0}_{m_0} D_0 + \underbrace{\bar{S}_1 S_0}_{m_1} D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

43



$$2 = \log_2(4)$$

$$2^2 = 4$$

 


S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3


$$3 = \log_2(8) \Rightarrow 2^3 = 8$$

  

 Example 6.1. Design a circuit for $Y = \underline{A\bar{B}} + \bar{B}\bar{C} + \bar{A}BC$ using a 8:1 MUX.




A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

 


Remark 6.1. A $2^N : 1$ MUX can be used to program any N -input logic function.

 Example 6.2. Design a circuit for $Y = \underline{A\bar{B}} + \bar{B}\bar{C} + \bar{A}BC$ using a 4:1 MUX and NOT gates only.





S1	S0	D0
0	0	1

$$Y = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

 

Remark 6.2. A $2^{N-1} : 1$ MUX can be used to program any N -input logic function, if we use literals on the input side.

Example 6.3. Design a circuit for $Y = \bar{A}C + \bar{A}B + B\bar{D}$ using a 8:1 MUX and NOT gates only. Also design using 4:1 MUX and other gates. fewest gates.

  


Problem 6.1. (15 marks [1, Ex-2.42]) Implement the function $Y = BC + \bar{A}\bar{B}\bar{C} + B\bar{C}$ using

1. an 8:1 multiplexer
2. a 4:1 multiplexer and no other gates
3. a 2:1 multiplexer, one OR gate, and an inverter

6.3 Encoders and Decoders

 
Example 6.4. Draw the symbol and the truth table for 2:4 decoder. Also write the logic expressions.



I_1	I_0	O_3	O_2	O_1	O_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$O_3 = m_3 = I_1 I_0 \quad O_1 = \bar{I}_1 I_0$$
 
$$O_2 = m_2 = I_1 \bar{I}_0 \quad O_0 = \bar{I}_1 \bar{I}_0$$



$$Y = BC + \bar{A}\bar{B}\bar{C} + B\bar{C}$$

Truth table for the 2:1 multiplexer:

	A		
Y	0	1	1
C	0	1	1

Red boxes highlight the first and third columns (C=0 and C=1). Blue boxes highlight the second and third rows (A=1 and A=0). Labels D_0 (red) and D_1 (blue) are placed below the columns.


$$Y = D_0 \text{ when } B=0$$

Truth table for the condition $Y = D_0$ when $B=0$:

	A	
Y	1	0
C	0	0

$$\begin{aligned} D_0 &= \bar{A}\bar{C} \\ &= \overline{(\overline{\bar{A}\bar{C}})} \\ &= \overline{A+C} \end{aligned}$$

$$f = \bar{f}$$

 


Example 6.5. Draw the symbol and the truth table for 3:8 decoder, 4:16 decoder and $N : 2^N$ decoder. Also write the logic expressions.



Example 6.6. Design a circuit for a XOR gate using a 2:4 decoder and an OR gate.

$$Y = A\bar{B} + \bar{A}B$$

$m_2 \quad m_1$

 


  Example 6.7. Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 3:8 decoder and an OR gate.



6.3.1 (Priority) Encoders

 Example 6.8. Draw symbol and truth table for a 4:2 priority encoder.



$I_7 > \dots > I_0$	O_2	O_1	O_0	E_n
1 x x x ... x	1	1	1	1
0 1 x x ... x	1	1	0	1
...				
0 0 ... 1	0	0	0	1
0 0 0 ... 0	0	0	0	0

$E_n = 0$

Example 6.9. Draw symbol and truth table for a 8:3 priority encoder.